

- $1 \text{ e} = 1.602 \times 10^{-19} \text{ C} \Leftrightarrow 1 \text{ C} = 6.24 \times 10^{18} \text{ e}$


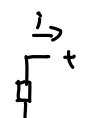
- $i = \frac{dq}{dt}$

$$Q = \int_{t_0}^t i \, dt$$

-  $b - a = -qV$


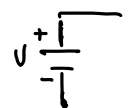
- $p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = v i$

- current enters $\begin{cases} \text{positive terminal of an element} \\ \text{negative} \end{cases} \quad \begin{aligned} p &= +vi \\ p &= -vi \end{aligned}$


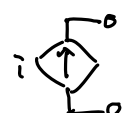
-  absorb  supply.

- conservation of energy $\sum p = 0$.

- $w = \int_{t_0}^t p \, dt = \int_{t_0}^t v i \, dt$

-  AC/DC  DC only
independent voltage source

 independent current source

-  dependent voltage source  current source

- $V = iR$ for PSC 提供能量

$V = -iR$ for ASC 吸收能量

- $p = vi = i^2 R = \frac{v^2}{R} = \frac{i^2}{G} = v^2 G \quad i = vG \quad G = \frac{1}{R} \text{ conductance}$

- b branch (支路) n nodes (节点) m meshes (回路)

$$b = m + n - 1$$


- Kirchhoff's current law (KCL): 过-节点 $\sum i = 0$. $\sum I_{\text{进}} = \sum I_{\text{出}}$

voltage law (KVL): sum of all voltages around a closed path (or

loop) is zero. $\sum U_{\text{drops}} = \sum U_{\text{rises}}$.

- Principle of voltage division: $V_n = \frac{R_n}{\sum_{n=1}^N R_n} V$
- current division: $i_n = \frac{G_n}{\sum_{n=1}^N G_n} i$

Wye - Delta Transformations

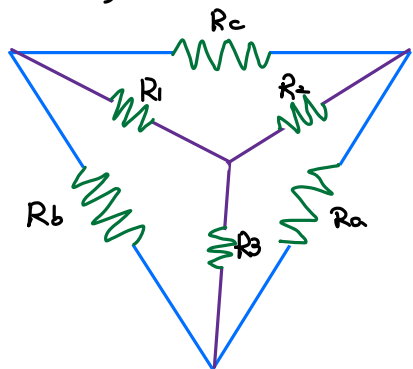

① $\pi \rightarrow Y$
Delta \Rightarrow Wye

$$\begin{cases} R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \\ R_2 = \frac{R_a R_c}{R_a + R_b + R_c} \\ R_3 = \frac{R_a R_b}{R_a + R_b + R_c} \end{cases}$$

② Wye \Rightarrow Delta $Y \rightarrow \pi$

$$\begin{cases} R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \\ R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\ R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \end{cases}$$

L3. Nodal Analysis

- circuit with only independent current sources. N nonreference nodes.

$$\begin{bmatrix} G_{11} & G_{12} & \vdots & G_{1N} \\ G_{21} & G_{22} & \vdots & G_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ G_{N1} & G_{N2} & \vdots & G_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{bmatrix}$$

G_{NN} = sum of conductances connected to node k

G_{kj} = 负的 k, j 间 conductances 之和

i_k = independent current sources 之和, 流入为正

- 若有 Voltage sources

* 1 两 nonreference nodes 间的电压源称 supernode (见 L3, P 37)
与此 node 平行的 elements 也合并

Mesh Analysis (只用于平面电路)

- circuit with only independent current sources. N nonreference nodes.

$$\begin{bmatrix} R_{11} & R_{12} & \vdots & R_{1N} \\ R_{21} & R_{22} & \vdots & R_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ R_{N1} & R_{N2} & \vdots & R_{NN} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{bmatrix}$$

$R_{NN} = \text{sum of resistances in mesh } k$

$R_{kj} = \text{负的 } k, j \text{ 间 resistances 之和}$

$V_k = \text{顺时针电压源之和, 电压上升为正}$

2. 若有 current source

① current source 只在一个 mesh, 则为 mesh current (L_3, P_3)

② c.s. 在两 mesh 间, 为 supermesh (L_3, P_3)

用法: nodal analysis { 多并联, 电流源, supernodes
node voltage required
node 少

mesh analysis { 多串联, 电压源, supermesh
branch-mesh currents required
mesh 少


L4 1. Superposition 叠加.

多个 independent sources 可分别求其 contribution.

dependent sources 不可分离出来

eg 见 L4 / P21

2. Source Transformation

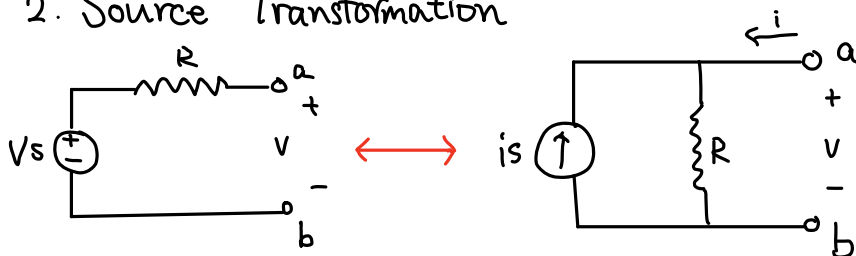

$$V_s = i_s R \quad \text{or} \quad i_s = \frac{V_s}{R}$$

3. Thevenin's Theorem

① network has no dependent sources: turn off all independent sources.


R_{th} is equivalent resistance between a & b.

② network has dependent sources: turn off all independent sources. apply a voltage source V_o (or current source i_o) at terminal a & b and determine the resulting current i_o . $R_{th} = \frac{V_o}{i_o}$.


4. 诺顿定理

二端电路可用电流源 I_N 和与之并联的电阻 R_N 构成的等效电路替代. I_N 流入端口的短路电流, R_N 独立电流源关闭时端口的等效电阻.

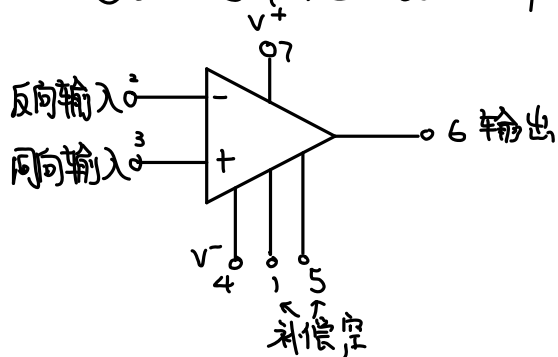
(5) 运算放大器 (operational amplifier, op amp)



供电电路

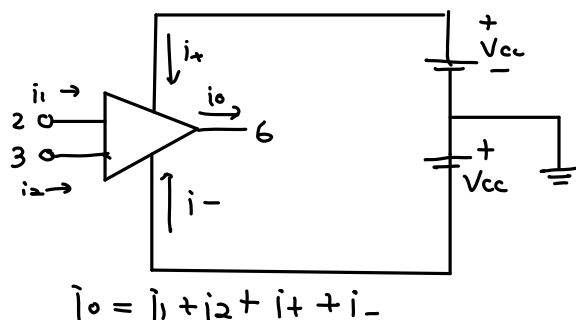

非理想运放等效图:

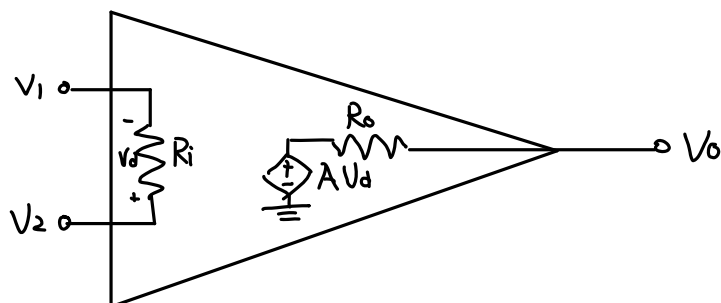

$$V_d = V_2 - V_1$$


$$V_o = AV_d = A(V_2 - V_1)$$

A 称为 开环电压增益

输出电压和输入电压之比称 闭环增益

输出电压值不超过 $|V_{cc}|$

V_{cc} ↑ 正饱和区

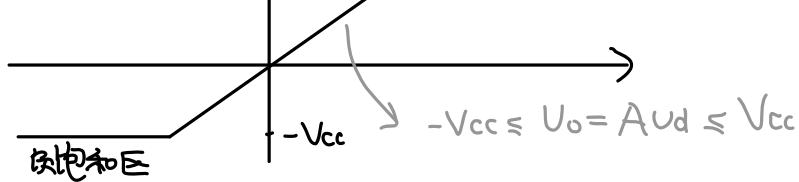

• 理想运算放大器



- 特点:
1. 开环增益无穷大 $A \approx \infty$
 2. 输入电阻无穷大 $R_i \approx \infty$
 3. 输出电阻为零 $R_o \approx 0$

- ∴ 性质:
1. 两输入电流均为零 $i_1 = 0 \quad i_2 = 0$
 2. 两输入端电压差为零 $U_d = U_2 - U_1 = 0 \quad U_1 = U_2$

• 反向放大器 Inverting amplifier

同向输入端接地, U_i 通过电阻 R_1 接入反向输入端. 反馈电阻 R_f 接在反向输入端与输出端之间.

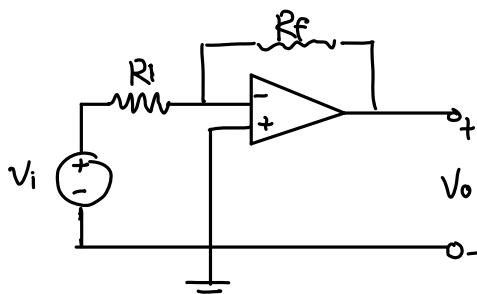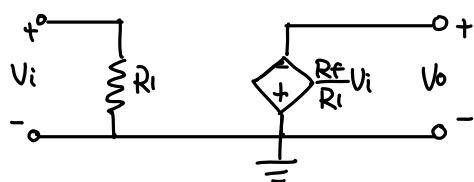
有 $U_o = -\frac{R_f}{R_1} U_i$ 电压增益 $A = \frac{U_o}{U_i} = -\frac{R_f}{R_1}$




• 同向放大器 Noninverting amplifier

输入电压 U_i 直接与同向输入端相连, 电阻 R_1 接在反向输入端与地之间.

$U_o = (1 + \frac{R_f}{R_1}) U_i$

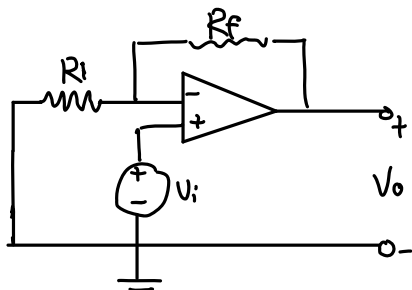

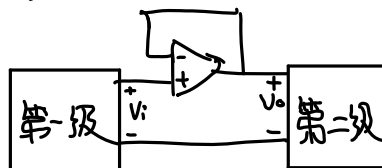
若 $R_f = 0$ 或 $R_1 = \infty$, $A = 1$. 电压跟踪器 ($U_o = U_i$)



• 加法放大器 Summing amplifier


将多个输入合并，在输出端产生这些输入加权和的运放，
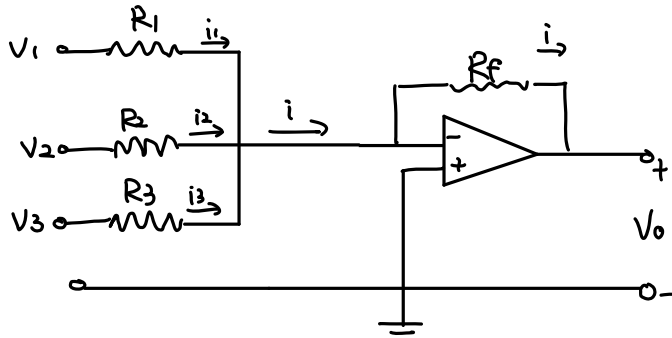
$$U_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} U_2 + \frac{R_f}{R_3} U_3 \right)$$



• 差分放大器 Difference amplifier

只对两输入信号差值进行放大和抑制共模信号的器件

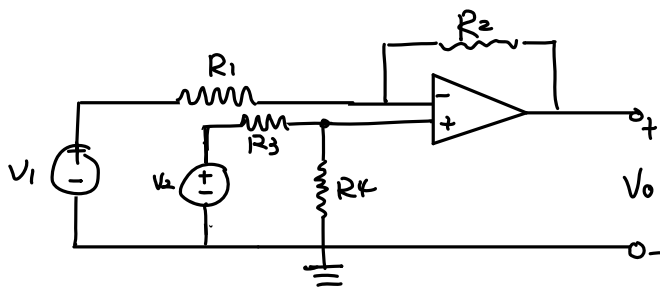

$$V_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} V_2 - \frac{R_2}{R_1} V_1$$

$$V_1 = V_2 \text{ 时 } V_o = 0 \text{ 需要 } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\therefore \text{差分放大器 } V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

若 $R_2 = R_1$ 且 $R_3 = R_4$ ，则为减法器

$$V_o = V_2 - V_1$$